

National University of Singapore
Department of Electrical & Computer Engineering
EE-4502: Electric Drives and Control
Tutorial - 3 (DC Motor Drives - Solution)
Year 2021-22

1. If we neglect armature copper loss $\Rightarrow (R_a \approx 0)$. Thus, we have

$$V_a = E_a + I_a \times R_a \simeq E_a (= k\phi\omega_m) \Rightarrow \omega_m = \frac{V_a}{k\phi}$$

$$T_{em} = k\phi I_a \Rightarrow I_a = \frac{T_{em}}{k\phi}$$

$$I_{a,rated} = 500 \text{ A and } N_{rated} = 800 \text{ rpm}$$

- (a) Load torque is maintained constant i.e. $T_{load} = \text{const.}$

$$\omega_m = \frac{V_a}{k\phi} = \frac{0.5 \text{ pu}}{0.8 \text{ pu}} \times 800 \text{ rpm} = 500 \text{ rpm}$$

$$T_{em} = T_{load} = \text{const.} \rightarrow I_a = \frac{1}{k\phi} \times 500 \text{ A} = 625 \text{ A}$$

- (b) Load torque is maintained constant i.e. $T_{load} \propto \omega_m^2$

$$\omega_m = \frac{V_a}{k\phi} = \frac{0.5 \text{ pu}}{0.8 \text{ pu}} \times 800 \text{ rpm} = 500 \text{ rpm}$$

$$T_{em} = T_{load} \propto \omega_m^2 \rightarrow I_a = \frac{1}{0.8} \times 0.625^2 \times 500 \text{ A} = 244.14 \text{ A}$$

2. The parameters given are:

$$V_{a,rated} = 250 \text{ V}, N_{rated} = 500 \text{ rpm}, R_a = 0.13 \Omega, I_{a,rated} = 60 \text{ A}$$

At rated operating conditions, the back-emf constant is:

$$k_E = \frac{V_a - I_a \times R_a}{\omega_m} = \frac{250 \text{ V} - 60 \text{ A} \times 0.13 \Omega}{\left(\frac{2\pi}{60}\right) \times 500 \text{ rpm}} = 4.62 \text{ V/(rad/s)}$$

- (a) At rated braking torque, we have

$$V_a = E_a + (-I_a) \times R_a \Rightarrow 250 \text{ V} = E_a - 60 \text{ A} \times 0.13 \Omega \Rightarrow E_a = 257.8 \text{ V}$$

$$N = \frac{E_a}{k_E} = \frac{257.8}{4.62} \times \frac{60}{2\pi} = 532.85 \text{ rpm}$$

(b) Under dynamic braking, we have $V_a = 0 \text{ V}$ and external resistance, R_{ext} is connected in series with the armature to limit the armature current to twice its rated value.

$$V_a = E_a + (-I_a) \times (R_a + R_{ext}) \Rightarrow 0 \text{ V} = 242.2 \text{ V} - (60 \times 2 \text{ A}) \times (0.13 + R_{ext}) \Omega$$

$$R_{ext} = 1.9 \Omega$$

At rated braking torque we have,

$$V_a = E_a + (-I_a) \times (R_a + R_{ext}) \Rightarrow 0 \text{ V} = E_a - 60 \text{ A} \times (0.13 + 1.9) \Omega$$

$$E_a = 121.2 \text{ V} \Rightarrow N = \frac{E_a}{k_E} = \frac{121.2}{4.62} \times \frac{60}{2\pi} = 250.5 \text{ rpm}$$

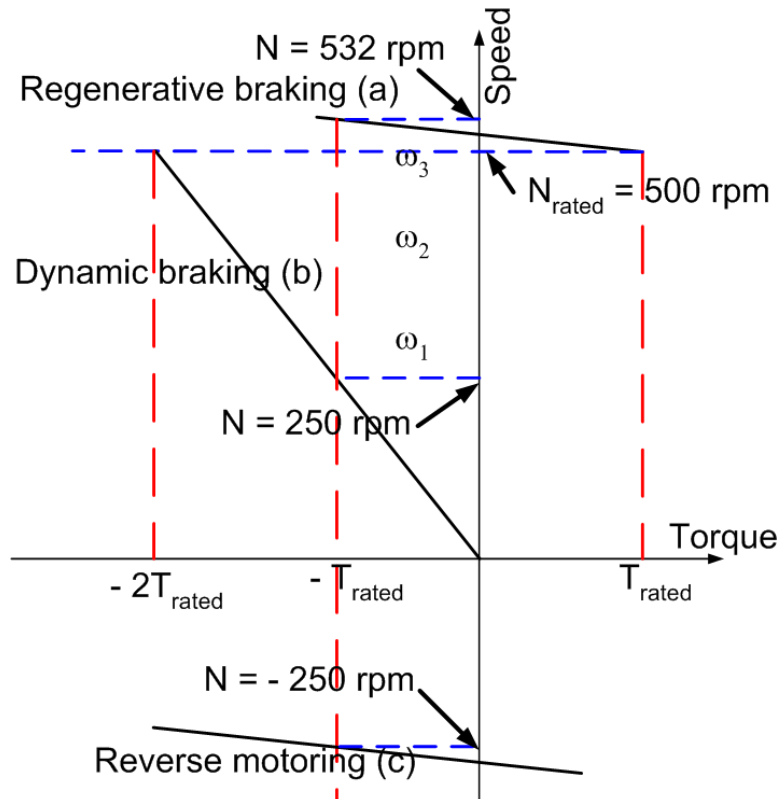


Figure 1:

(c)

$$V_a = E_a + (I_a) \times R_a = \left(-4.62 \times \frac{2\pi}{60} \times \frac{500}{2}\right) + (-60 \text{ A}) \times 0.13 = -128.9 \text{ V}$$

3. The parameters given are:

$$V_{dc} = 500 \text{ V}, I_{a, \text{rated}} = 20 \text{ A}, R_a = 0.5 \Omega,$$

$$L_a = 20 \text{ mH}, \text{ and } f_s = 1000 \text{ Hz}$$

At rated operating conditions, the back-emf constant is:

$$k_E = \frac{V_a - I_a \times R_a}{\omega_m} = \frac{500 \text{ V} - 20 \text{ A} \times 0.5 \Omega}{\left(\frac{2\pi}{60}\right) \times 1170 \text{ rpm}} = 4.00 \text{ V/(rad/s)}$$

(a) The back-emf at 800 rpm is:

$$E_a = 4 \times \left[\left(\frac{2\pi}{60}\right) \times 800\right] = 335.1 \text{ V}$$

The corresponding armature voltage is

$$V_a = 335.1 \text{ V} + 20 \text{ A} \times 0.5 \Omega = 345.1 \text{ V}$$

Thus, the duty-cycle of the chopper is

$$D = \frac{345.1 \text{ V}}{500 \text{ V}} = 0.69$$

(b) The corresponding armature current is as shown in Fig. 2.

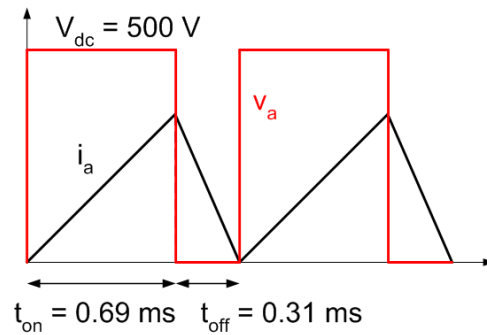


Figure 2:

The corresponding voltage eqn. during the current rise period is

$$v_a = i_a \times R_a + L_a \times \left(\frac{di_a}{dt}\right) + e_a$$

$$\Rightarrow 500 \text{ V} = i_a \times 0.5 \Omega + 20.0 \times 10^{-3} \times \left(\frac{di_a}{dt}\right) + 4 \times \left[\left(\frac{2\pi}{60}\right) \times 800\right]$$

Assuming the speed remains constant and solving the differential equation we get,

$$i_a(t) = 329.8 (1 - \exp(-t/0.04)) \text{ A}$$

At the end of the ON period ($t = 0.69 \text{ ms}$), we have,

$$i_a(t = 0.69 \text{ ms}) = 329.8 (1 - \exp(-0.00069/0.04)) \text{ A} = 5.64 \text{ A}$$

Assuming that the rise of the current is linear, the average armature current for this operating condition is

$$I_a = \frac{1}{2} \times 5.64 \text{ A} = 2.82 \text{ A}$$

This gives rise to a torque of

$$T_{em} = k_T \times I_a = 4.0 \times 2.82 \text{ A} = 11.3 \text{ N.m}$$

4. The parameters given are:

$$V_{rated} = 230 \text{ V}, I_{a,rated} = 90 \text{ A}, N_{rated} = 500 \text{ rpm}, R_a = 0.115 \Omega,$$

$$L_a = 11 \text{ mH}, V_s = 230 \text{ V DC}, \text{ and } f_s = 400 \text{ Hz}$$

Under rated condition, we have

$$E_{a,rated} = 230 \text{ V} - 90.0 \text{ A} \times 0.115 \Omega = 219.65 \text{ V}, k\phi_{rated} = \frac{219.65 \text{ V}}{500} = 0.439 \text{ V/rpm}$$

(a) For $\delta = 0.5$ and $I_a = 90 \text{ A}$, we have

$$E_a = 0.5 \times 230 \text{ V} - 90 \text{ A} \times 0.115 \Omega = 104.7 \text{ V} \Rightarrow N = \frac{104.7 \text{ V}}{219.65 \text{ V}} \times 500 = 238.2 \text{ rpm}$$

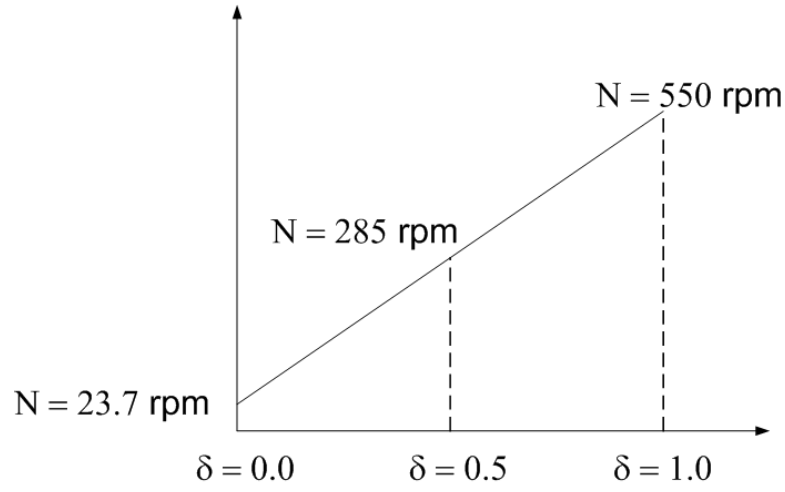


Figure 3:

(b) For braking at rated torque $I_a = -90 A$. We have

$$\begin{aligned}\delta \times V_s &= E_a + I_a \times R_a \\ \delta \times 230 &= 0.439 \times N - 90 \times 0.115 \\ \delta &= 0.0019 \times N - 0.045\end{aligned}$$

For $\delta = 0$, we have

$$0 = 0.0019 \times N_{min} - 0.045 \Rightarrow N_{min} = 23.7 \text{ rpm}$$

5. The parameters given are:

$$R_a = 0.4 \Omega, L_a = 1.5 \text{ mH}, k_E = k_T = 0.5, J_m = 0.02 \text{ kg.m}^2,$$

$$T_{rated} = 4 \text{ N.m}, V_s = 200 \text{ V}, f_s = 25 \text{ kHz}$$

At $N = 1500 \text{ rpm}$, we have

$$V_a = \frac{2\pi}{60} \times 1500 \times 0.5 + \frac{3}{0.5} \times 0.4 = 80.95 \text{ V}$$

Duty-cycle

$$D = \frac{V_a}{V_s} = \frac{80.95}{200} = 0.4$$

Turn-on time

$$t_{on} = D \times T_s = 0.4 \times \frac{1}{25 \text{ kHz}} = 16 \mu\text{s}$$

Turn-off time

$$t_{off} = T_s - t_{on} = 40 \mu s - 16 \mu s = 24 \mu s$$

The average armature current is

$$I_a = \frac{T}{k_T} = \frac{3 \text{ N.m}}{0.5 \text{ N.m/A}} = 6 \text{ A}$$

During the on-period we have

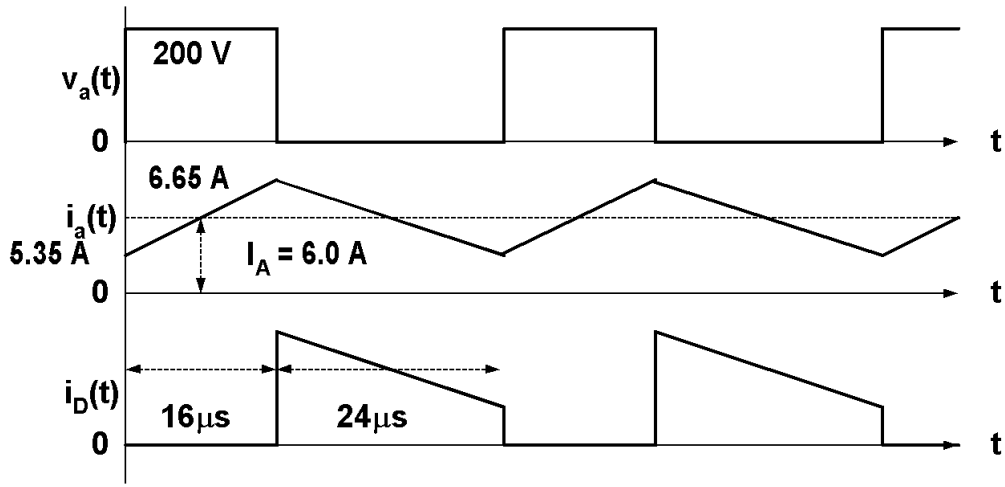


Figure 4:

$$\begin{aligned} v_a(t) &= e_a(t) + i_a(t) \times R_a + L_a \frac{di_a}{dt} \\ &\approx e_a(t) + L_a \frac{di_a}{dt} \\ 200 \text{ V} - 157.1 \times 0.5 &= 1.5 \times 10^{-3} \frac{di_a}{16 \mu s} \\ di_a &= 1.3 \text{ A} \end{aligned}$$

Thus, we have

$$i_{a,min} = 6 \text{ A} - \frac{1.3 \text{ A}}{2} = 5.35 \text{ A}, i_{a,max} = 6 \text{ A} + \frac{1.3 \text{ A}}{2} = 6.65 \text{ A}$$

(b) At 1200 rpm, we have

$$V_a = \frac{2\pi}{60} \times 1200 \times 0.5 + (-10 \text{ A}) \times 0.5 = 57.83 \text{ V}$$

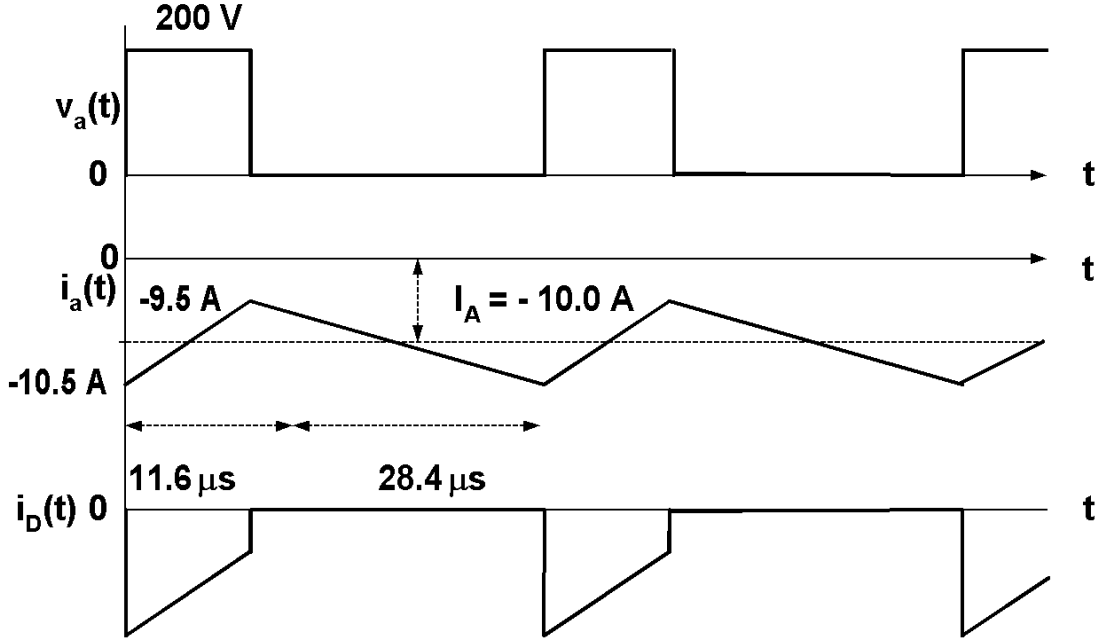


Figure 5:

Duty-cycle

$$D = \frac{V_a}{V_s} = \frac{57.83}{200} = 0.289$$

Turn-on time

$$t_{on} = D \times T_s = 0.289 \times \frac{1}{25 \text{ kHz}} = 11.6 \mu s$$

Turn-off time

$$t_{off} = T_s - t_{on} = 40 \mu s - 16 \mu s = 28.4 \mu s$$

During the period when the diode is ON, we have

$$\begin{aligned} v_a(t) &= e_a(t) + i_a(t) \times R_a + L_a \frac{di_a}{dt} \\ &\approx e_a(t) + L_a \frac{di_a}{dt} \\ 200 \text{ V} - 125.7 \times 0.5 &= 1.5 \times 10^{-3} \frac{di_a}{11.6 \mu s} \\ di_a &= 1.06 \text{ A} \end{aligned}$$

Thus, we have

$$i_{a,min} = -10.0 \text{ A} - \frac{1.06 \text{ A}}{2} = -10.53 \text{ A}, i_{a,max} = -10.0 \text{ A} + \frac{1.06 \text{ A}}{2} = -9.47 \text{ A}$$

6. The parameters given are:

$$V_{dc} = 200 \text{ V}, T_l = c\omega_m^2, R_a = 0.5 \Omega, k\phi = 0.6 \text{ N.m/A}$$

For $T_{l1} = 9 \text{ N.m}$, we have

$$I_{a1} = \frac{9}{0.6} = 15 \text{ A}$$

For $N_2 = 500 \text{ rpm}$

$$T_{l2} = 9 \times \left(\frac{500}{1000} \right)^2 = 2.25 \text{ N.m}, I_{a2} = \frac{2.25}{0.6} = 3.75 \text{ A}$$

At 500 rpm,

$$E_{a2} = k\phi\omega_{m2} = 0.6 \times \frac{2\pi}{60} \times 500 = 31.4 \text{ V}$$

Thus,

$$V_{a2} = 31.4 \text{ V} + 3.75 \text{ A} \times 0.5 \Omega = 33.3 \text{ V} \Rightarrow \delta_2 = \frac{33.3}{200} = 0.17$$

For $N_3 = 200 \text{ rpm}$

$$T_{l3} = 9 \times \left(\frac{200}{1000} \right)^2 = 0.36 \text{ N.m}, I_{a3} = \frac{0.36}{0.6} = 0.6 \text{ A}$$

At 200 rpm,

$$E_{a3} = k\phi\omega_{m3} = 0.6 \times \frac{2\pi}{60} \times 200 = 12.57 \text{ V}$$

Thus,

$$V_{a3} = 12.57 \text{ V} + 0.6 \text{ A} \times 0.5 \Omega = 12.87 \text{ V} \Rightarrow \delta_3 = \frac{12.9}{200} = 0.064$$

Thus, the range over which δ varies is $\boxed{0.064 < \delta < 0.17}$.

7. The parameters given are

$$V_{a,rated} = 220 \text{ V}, N_{rated} = 1750 \text{ rpm}, N = 1500 \text{ rpm}, R_a = 0.067 \Omega,$$

$$V_{dc} = 240 \text{ V}, f_s = 400 \text{ Hz}, k\phi = 1.28 \text{ N.m/A}, i_{a,max} = 290 \text{ A}$$

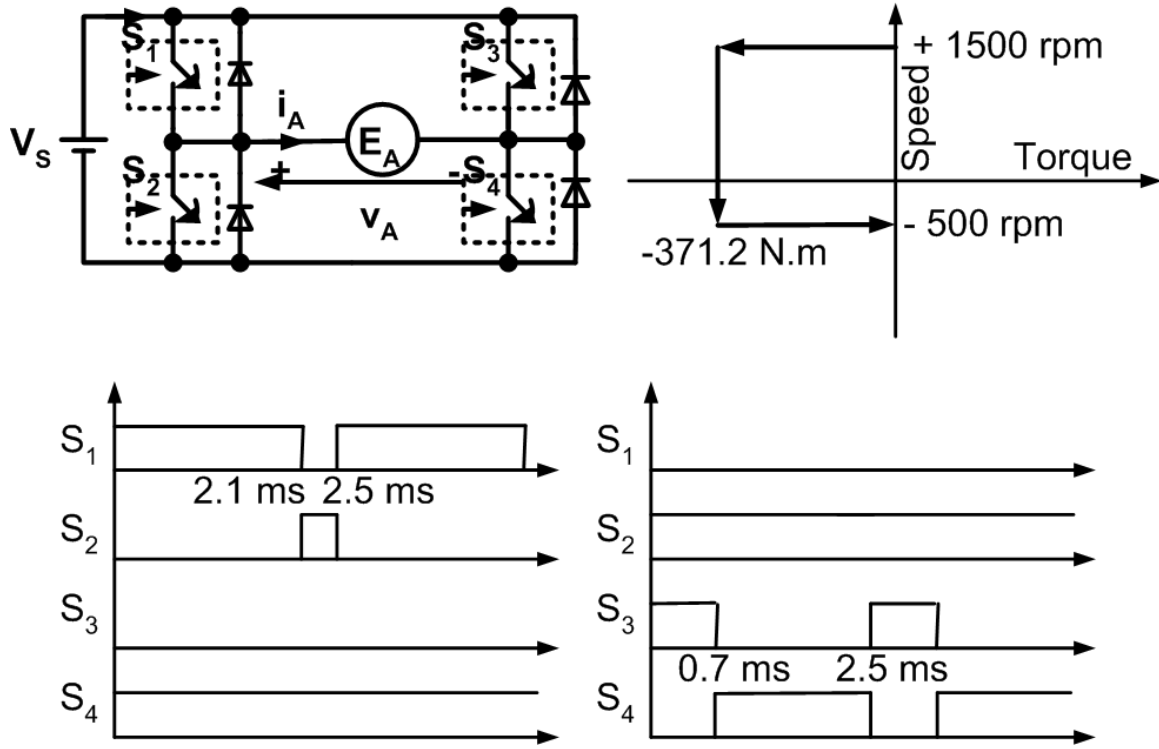


Figure 6: Chopper Circuit

At $N = 1500 \text{ rpm}$ we have

$$\begin{aligned}
 E_a &= 1.28 \times \frac{2\pi}{60} \times 1500 = 201.1 \text{ V} \\
 \Rightarrow V_a &= 201.1 + 0 \times 0.067 \Omega = 201.1 \text{ V} \\
 \Rightarrow t_{ON} &= \left(\frac{201.1}{240} \right) \times \left(\frac{1}{400} \right) = 2.1 \text{ ms}
 \end{aligned}$$

Since the operation is in quadrant-I, switch S_4 is permanently ON while switch S_3 is completely OFF. The corresponding gating signals for all the switches are as shown in Fig. 6.

For operations at 1500 rpm in quadrant-II just after deceleration begins, at $N = 1500 \text{ rpm}$ we have

$$\begin{aligned}
 E_a &= 1.28 \times \frac{2\pi}{60} \times (1500) = 201.1 \text{ V} \\
 \Rightarrow V_a &= 201.1 - 290 \text{ A} \times 0.067 \Omega = 181.67 \text{ V} \\
 \Rightarrow t_{ON} &= \left(\frac{181.67}{240} \right) \times \left(\frac{1}{400} \right) = 1.9 \text{ ms}
 \end{aligned}$$

For operations at -500 rpm in quadrant-III, we have At $N = -500 \text{ rpm}$ we have

$$\begin{aligned}E_a &= 1.28 \times \frac{2\pi}{60} \times (-500) = -67.03 \text{ V} \\ \Rightarrow V_a &= -67.03 + 0 \times 0.067 \Omega = -67.03 \text{ V} \\ \Rightarrow t_{ON} &= \left(\frac{67.03}{240} \right) \times \left(\frac{1}{400} \right) = 0.7 \text{ ms}\end{aligned}$$

Since the operation is in quadrant-III, switch S_2 is permanently ON while switch S_1 is completely OFF. The corresponding gating signals for all the switches are as shown in Fig. 6.

— END —